



## Department of Electrical Engineering

Faculty Member: Qurat al Ain

Dated: February 29, 2024

Semester: 4<sup>th</sup>

Section: D

### EE215: ELECTRONIC DEVICES AND CIRCUITS

#### Lab 04: Small signal operation of pn-junction diodes

		PLO4/CLO4		PLO5/CLO5	PLO8/CLO6	PLO9/CLO7
Name	Reg. No	Viva /Quiz / Lab Performanc e  5 marks	Analysis of data in Lab Report  5 marks	Modern Tool Usage  5 marks	Ethics and Safety  5 marks	Individual and Teamwork  5 marks
Haseeb Umer	427442					
Hanzla Sajjad	403214					
Irfa Farooq	412564					



## Lab 04: Small signal operation of pn-junction diodes

### Objective: To Study the small signal analysis of diode circuits

1. The aim of this experiment is to investigate the diode small-signal AC model that was developed in class.

### EQUIPMENT REQUIRED

2. The following components and test equipment is required.
  - PN Diode (D1N4002 or any other diode of the same family)
  - Oscilloscope
  - Function Generator
  - Resistors
  - Capacitors
  - DC Power Supply

### The Experiment:

3. The experiment is broken down into three exercises. It involves the calculation of required parameters in the circuit given. Second exercise involves the simulation of the circuit on PSpice using OrCAD-Capture module. The third one involves the practical setup of this circuit and making required measurements, tabulation, and its analysis.

### Theory:

4. For a forward biased diode, the small-signal resistance is given by

$$r_d = \frac{nV_T}{I_{DQ}}$$



where  $V_T$  is the thermal voltage,  $n$  is the ideality factor, and  $I_{DQ}$  is the quiescent (DC) diode current.

The theory behind this experiment is outlined  
istics of a  $pn$  junction diode is


The  $i$ - $v$  character-

$$i_D = I_s \left[ e^{v_D/nV_T} - 1 \right],$$

where the ideality factor  $n$  is a number between 1 and 2. By definition, the small-signal resistance is the inverse of the slope of this  $i$ - $v$  curve evaluated at the Q-point. In other words,

$$\frac{1}{r_d} = \frac{d}{dv_D} \left[ I_s \left[ e^{v_D/nV_T} - 1 \right] \right] \bigg|_{v_D=V_{DQ}} = \frac{I_s e^{V_{DQ}/nV_T}}{nV_T} \simeq \frac{I_{DQ}}{nV_T},$$

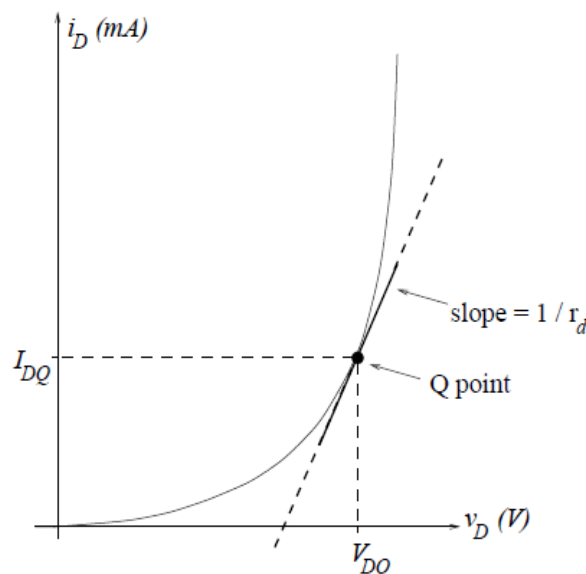since  $I_{DQ} \simeq I_s e^{V_{DQ}/nV_T}$  for a forward biased diode.





The diode small-signal AC model is a linear approximation to the exponential diode  $i-v$  curve around a DC operating point in the forward-bias region. Consider a diode in a circuit. The presence of the diode with its nonlinear  $i-v$  relationship poses a problem in analyzing the circuit. In general, the diode voltage and current may have both DC and AC components. The small-signal AC model may be used if


- (i) the diode is biased to a DC Q-point in the forward-bias region and
- (ii) the AC component of the diode voltage is small relative to  $nV_T$ .

The DC diode current and voltage (the Q-point) may be found using either a numerical method to solve the exponential  $i-v$  relationship or a simple piecewise linear model. Once the Q-point is found, AC variations around that Q-point can be considered to be approximately linear, provided they are small in amplitude. The AC diode current can then be considered to be linearly related to the AC diode voltage, and hence the diode can be modeled as a resistor with a resistance that is equal to the inverse of the slope of the  $i-v$  curve at the Q-point. The small-signal AC model begins to break down if the AC voltage across the diode exceeds  $nV_T$ . In this case distortions due to the diode nonlinearity become noticeable in the circuit.


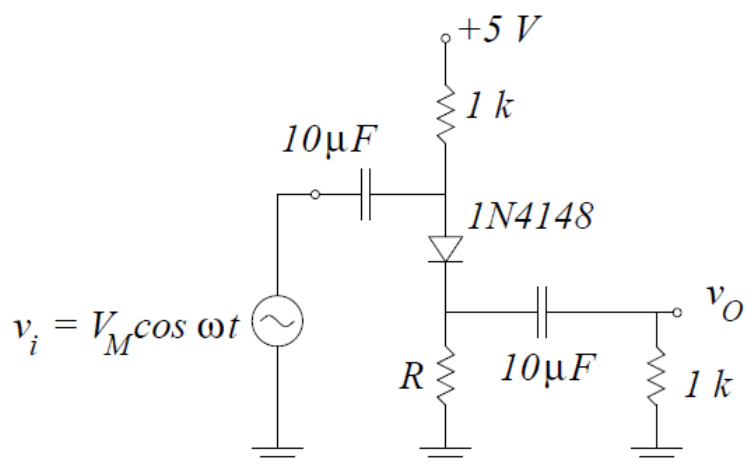
## Calculations:

In the laboratory, you will investigate the following circuit.



$$R = 4.7 \text{ k}\Omega, R = 68 \text{ k}\Omega$$

These  $R$  values will bias the diode at two different Q-points in the forward-bias region. The small-signal resistance  $r_d$  will therefore be different for different values of  $R$ .

For each value of  $R$ , perform the following steps. Assume that the coupling capacitors are short circuit at the frequency of operation. Also assume that the input voltage signal  $v_i$  is small enough so that  $v_d \ll nV_T$ . The ideality factor of 1N4148 diodes is 2.

1. Find the quiescent diode current  $I_{DQ}$  using a piecewise linear model with  $V_\gamma = 0.6 \text{ V}$ .
2. Determine the small-signal resistance  $r_d$  and draw the small-signal AC model for the circuit.



## Simulation:

Simulate the circuit using PSPICE. The diode is listed in PSPICE library as D1N4148. Use VSIN as the AC voltage source. First simulate using bias point analysis to find out all the DC voltages and currents and compare Q point with your calculations. Then use Time domain analysis to calculate small signal voltage gain using  $V_m = 50\text{mV}$  and  $f = 5\text{kHz}$ . Comment on your simulation results and attach screenshots of the graph obtained.

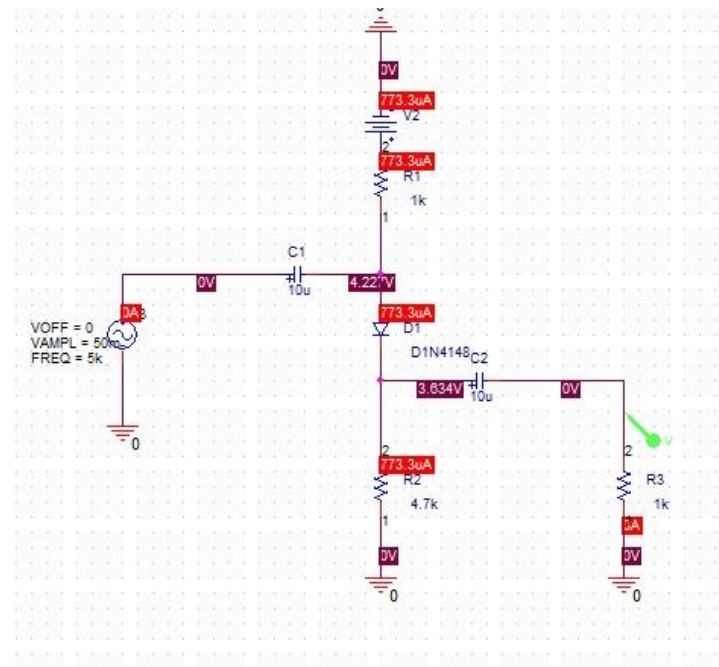


Figure 1: Hardware Simulation

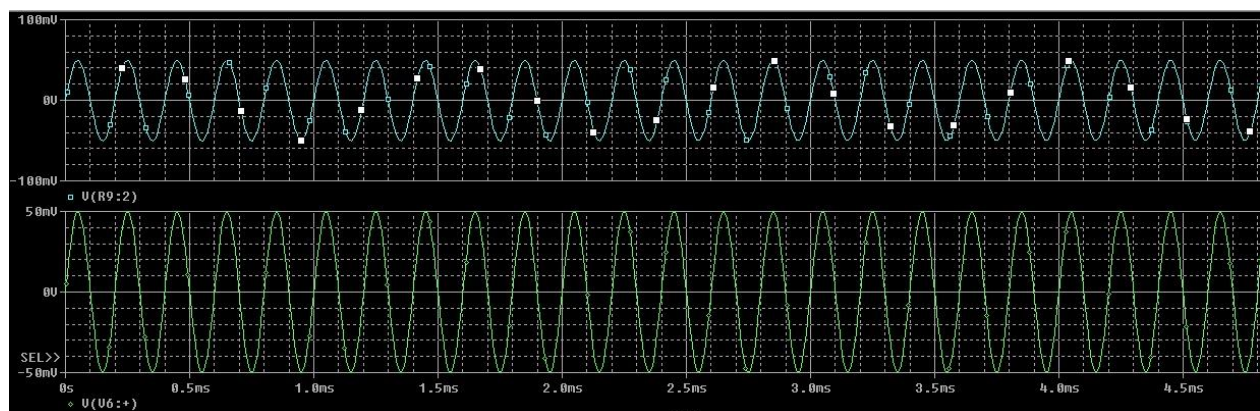


Figure 2: Voltage across input and Output using 4.7Kohm Resister



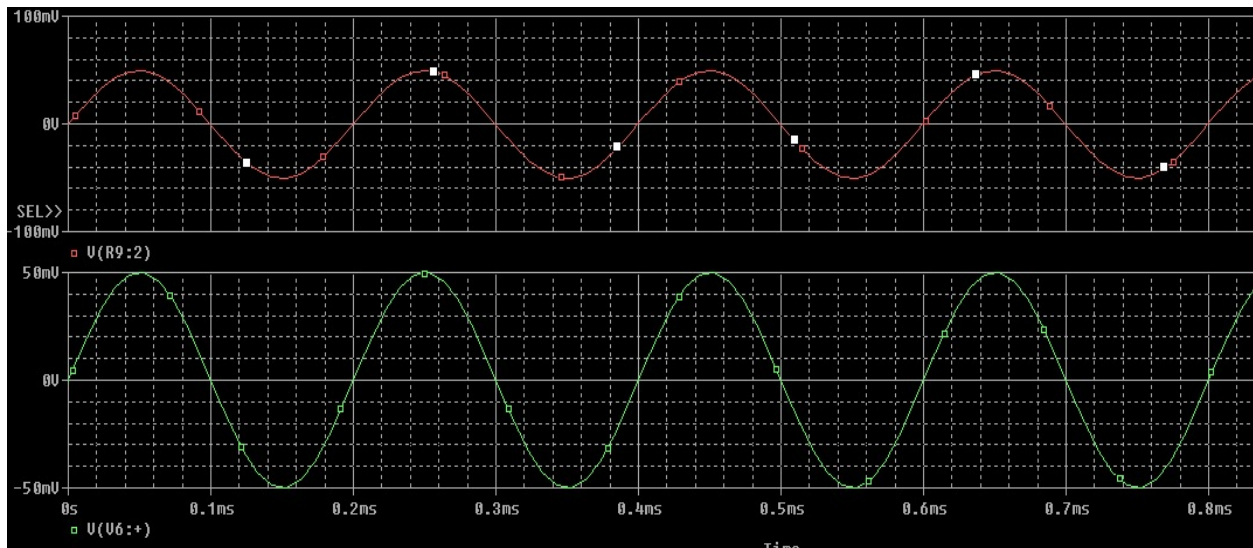


Figure 3: Voltage across Input and Output for 68KOhm Resistor

## Implementation:

Construct the circuit using the value of  $R$  given in your lab. (Note that the capacitors that you use here are electrolytic capacitors. Make sure to connect positive terminal of the capacitor towards the dc power supply. Set the signal generator frequency to 5kHz sinusoidal and amplitude to 100mV peak to peak.

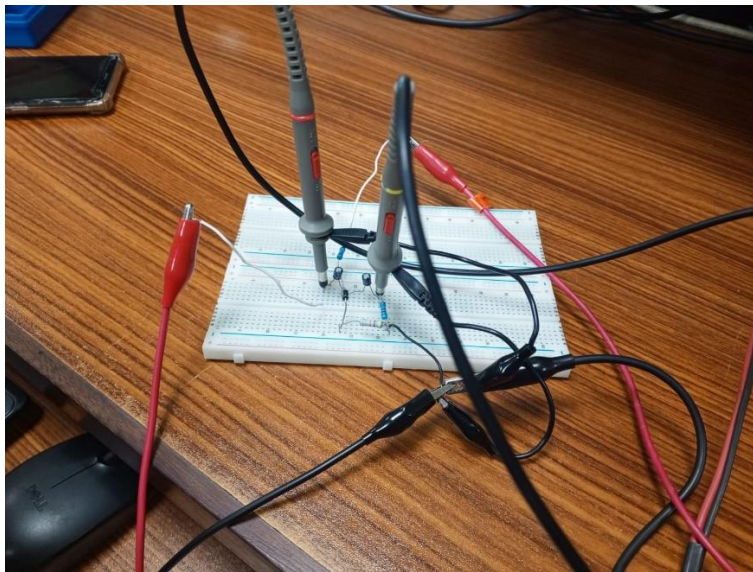


Figure 4: hardware Implementation



1. Turn off the signal generator. Measure the DC voltage drop (with a multimeter) across the  $1\text{ k}\Omega$  resistor that is connected to the DC supply. From your measurement, determine the quiescent diode current  $I_{DQ}$  and make sure that the diode is biased properly. Measure the DC voltage drop across the diode ( $V_{DQ}$ ) as well.

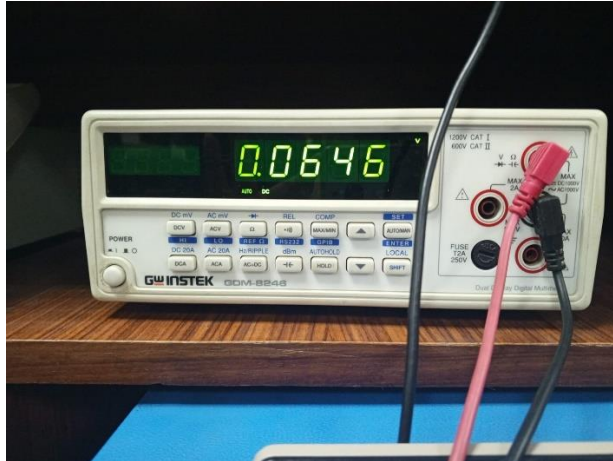


Figure 5: Voltage drop across  $68\text{ k}\Omega$

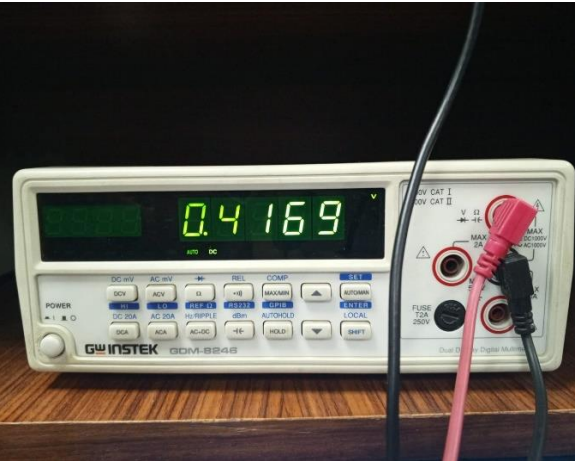


Figure 6: Voltage drop across Diode

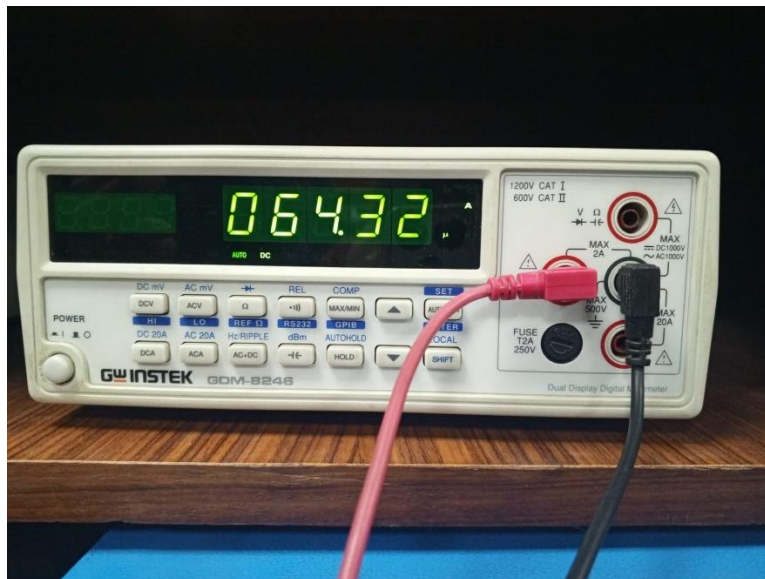


Figure 7: Current across Diode





2. Turn on the signal generator. Observe the input and output voltage waveforms on the oscilloscope on two separate channels. Measure the small-signal voltage gain  $A_v$ . Compare this with the value calculated in your preliminary work.

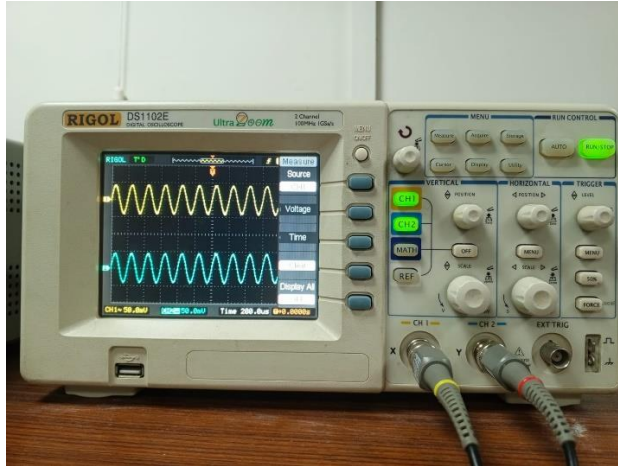


Figure 8: Sine Wave for 4.7kOhm Resistor

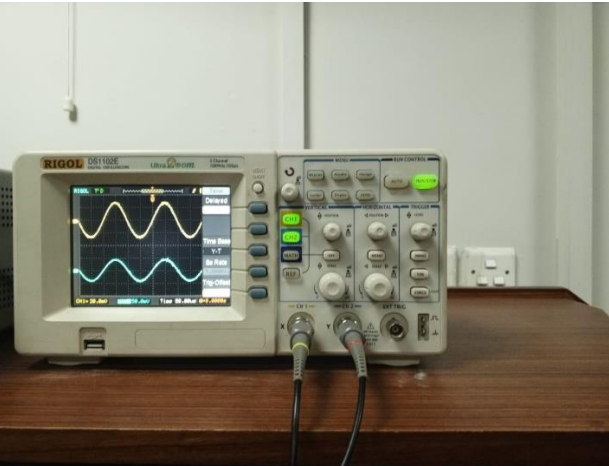


Figure 9: Sine Wave for 68kOhm Resistor

3. Increase the signal generator amplitude ( $V_M$ ) until you begin to see distortion at the output (output no longer sinusoidal). Note the input voltage when this occurs.

**Ans:** The output starts to distort from Sinusoidal wave when the input voltage exceeds 310mV.

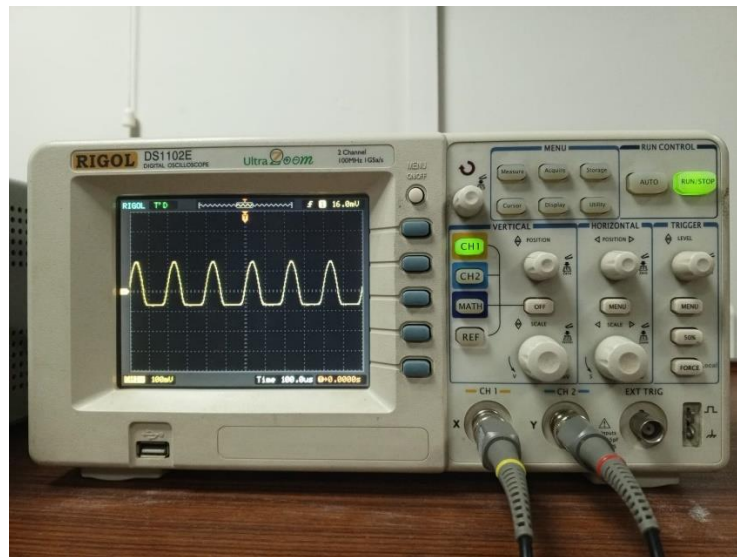


Figure 10: The Distorted Waveform



4. Put the oscilloscope into XY-mode to observe and record the input-output graph of this

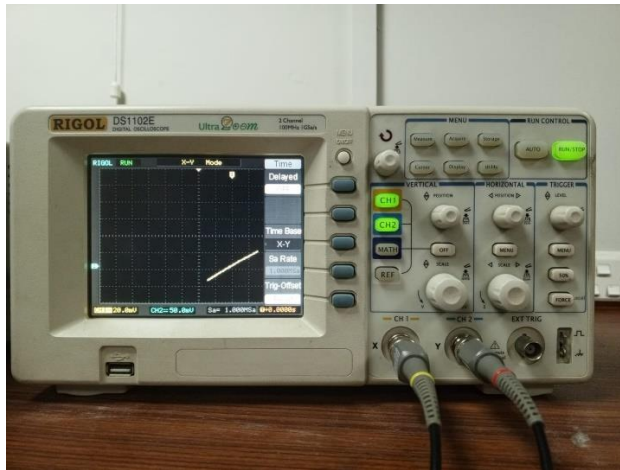


Figure 11: Output Graph for 4.7kOhm Resistor

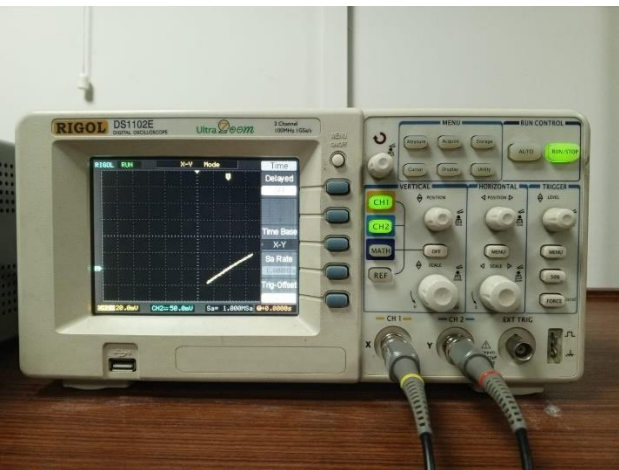


Figure 12: Output Graph for 68kOhm Resistor

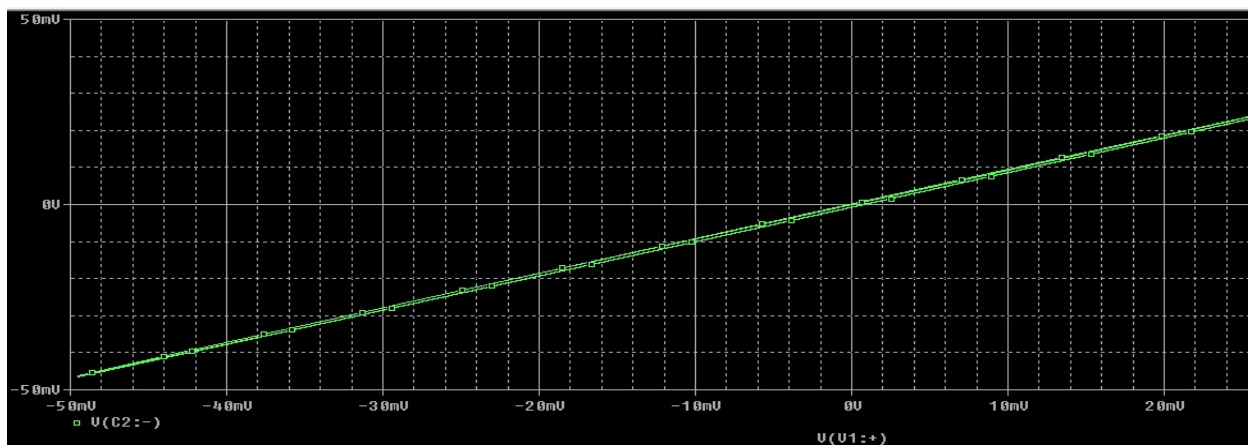


Figure 13: X-Y Graph for 4.7kOhm Resistor

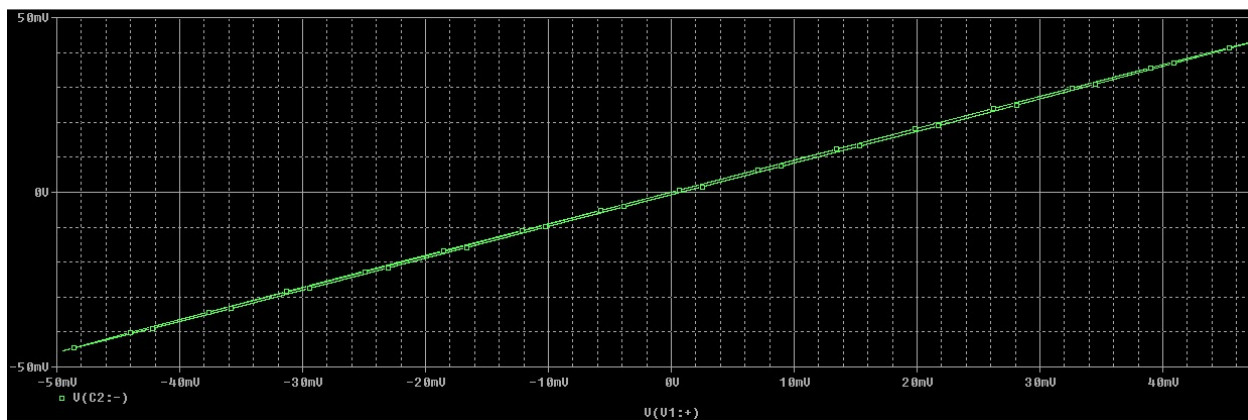


Figure 6: X-Y Graph for 68kOhm Resistor